

ELEMENTS OF COMPUTING



PRESENTED BY:

- 1.Shreya Arun-CB.SC.U4AIE23253
- 2.Varshitha Thilak Kumar-CB.SC.U4AIE23258
- 3.Siri Sanjana Singareddy-CB.SC.U4AIE23249

CEN, Amrita School of Artificial Intelligence,
Amrita Vishwa Vidyapeetham, Amritanagar P.O, Coimbatore-641112

OVERVIEW

PART-A:HACK CPU

- Introduction
- Design
- Implementation

PART-B:DESIGN AND IMPLEMENT SYNCHRONOUS DOWNCOUNTER FROM 0 TO 9

- Introduction
- Truth Table
- K-map
- Design
- Implementation
- Conclusion

INTRODUCTION


- The Hack platform is a **16-bit von Neumann machine**, designed to execute programs written in the Hack machine language.

To implement the Hack CPU,

- ALU chip capable of computing arithmetic/logical functions
- Set of registers
- Program counter, some additional gates designed to help decode, execute, and fetch instructions



ALU

 - We need a 16-bit Adder chip and a couple of logic gates including 16-bit Multiplexor, 16-bit NOT, 16-bit AND, 8-way OR, OR, and NOT



REGISTERS

  - 1. Data Register (D) : This register is used for storing data values.
- 2. Address Register (A): The A register serves three different purposes, depending on the context in which it is used: storing a data value, pointing at an address in the instruction memory, or pointing at an address in the data memory.
- 3. Program Counter (PC): This register holds the address of the next instruction to be executed.



MEMORY

- The architecture which include a 16-bit address space .It uses separate memory space for data (RAM) and instructions (ROM)

PC COUNTER

- Program Counter holds the memory address of the next instruction that would be executed.

ALU

HDL CODE

```
CHIP ALU {
    IN
        x[16], y[16], // 16-bit inputs
        zx, // zero the x input?
        nx, // negate the x input?
        zy, // zero the y input?
        ny, // negate the y input?
        f, // compute out = x + y (if 1) or x & y (if 0)
        no; // negate the out output?

    OUT
        out[16], // 16-bit output
        zr, // 1 if (out == 0), 0 otherwise
        ng; // 1 if (out < 0), 0 otherwise

PARTS:
    Mux16(a=x,b=false,sel=zx,out=xz);
    Mux16(a=y,b=false,sel=zy,out=yz);
    Not16(in=xz,out=negx);
    Not16(in=yz,out=negy);
    Mux16(a=xz,b=negx,sel=nx,out=xn);
    Mux16(a=yz,b=negy,sel=ny,out=yn);
    Add16(a=xn,b=yn,out=addxy);
    And16(a=xn,b=yn,out=andxy);
    Mux16(a=andxy,b=addxy,sel=f,out=fxxy);
    Not16(in=fxxy,out=notfxxy);
    Mux16(a=fxxy,b=notfxxy,sel=no,out=out,out[15]=ng,out[0..7]=lsb,out[8..15]=msb);
    Or8Way(in=lsb,out=or1);
    Or8Way(in=msb,out=or2);
    Or(a=or1,b=or2,out=or3);
    Not(in=or3,out=zr);
}
```

IMPLEMENTATION

Chip Name :

Time :

Input pins		Output pins	
Name	Value	Name	Value
x[16]	17	out[16]	19
y[16]	3	zr	0
zx	0	ng	0
nx	1		
zy	0		
ny	1		
f	0		
no	1		

HDL

```
// if (ny == 1) set y = !y
// if (f == 1) set out = x + y
// if (f == 0) set out = x & y
// if (no == 1) set out = !out
// if (out == 0) set zr = 1
// if (out < 0) set ng = 1

CHIP ALU {
    IN
        x[16], y[16], // 16-bit
        zx, // zero the x input?
        nx, // negate the x input?
        zy, // zero the y input?
        ny, // negate the y input?
```

Internal pins

Name	Value
negx[16]	-18
negy[16]	-4
xn[16]	-18
yn[16]	-4
addxy[16]	-22
andxy[16]	-20
fxxy[16]	-20
notfxxy[16]	19
lsb[8]	19
msb[8]	0
or1	1
or2	0
or3	1

```
set zy 0,
set ny 0,
set f 1,
set no 1,
eval,
output;

// Compute y - x
set zx 0,
set nx 0,
set zy 0,
set ny 1,
set f 1,
set no 1,
eval,
output;

// Compute x & y
set zx 0,
set nx 0,
set zy 0,
set ny 0,
set f 0,
set no 0,
eval,
output;

// Compute x | y
set zx 0,
set nx 1,
set zy 0,
set ny 1,
set f 0,
set no 1,
eval,
output;
```

End of script - Comparison ended successfully

BIT

IMPLEMENTATION

HDL CODE

```
CHIP Bit {
    IN in, load;
    OUT out;

    PARTS:
        // Put your code here:
        Mux(a=gayout, b=in, sel=load, out=a);
        DFF(in=a, out=out, out=gayout);
}
```

Chip Name : Bit (Clocked)Time : 107

Input pins		Output pins	
Name	Value	Name	Value
in	1	out	0
load	0		

HDL		Internal pins	
		Name	Value
<pre>* 1-bit register: * If load[t] == 1 then out[t+1] * else out does */ CHIP Bit { IN in, load; OUT out; PARTS: // Put your code here: Mux(a=dffOut, b=in, sel=load, out=m DFF(in=muxOut, out=dffOut, out=out }</pre>		dffOut	0
		muxOut	0

```
output;
tock,
output;

set in 1,
set load 0,
tick,
output;

tock,
output;

set in 1,
set load 0,
tick,
output;

tock,
output;

set in 1,
set load 0,
tick,
output;

tock,
output;

set in 1,
set load 0,
tick,
output;

tock,
output;
```


REGISTERS

HDL CODE

```
CHIP Register {
    IN in[16], load;
    OUT out[16];

    PARTS:
        // Put your code here:
        Bit(in=in[0],load=load,out=out[0]);
        Bit(in=in[1],load=load,out=out[1]);
        Bit(in=in[2],load=load,out=out[2]);
        Bit(in=in[3],load=load,out=out[3]);
        Bit(in=in[4],load=load,out=out[4]);
        Bit(in=in[5],load=load,out=out[5]);
        Bit(in=in[6],load=load,out=out[6]);
        Bit(in=in[7],load=load,out=out[7]);
        Bit(in=in[8],load=load,out=out[8]);
        Bit(in=in[9],load=load,out=out[9]);
        Bit(in=in[10],load=load,out=out[10]);
        Bit(in=in[11],load=load,out=out[11]);
        Bit(in=in[12],load=load,out=out[12]);
        Bit(in=in[13],load=load,out=out[13]);
        Bit(in=in[14],load=load,out=out[14]);
        Bit(in=in[15],load=load,out=out[15]);
}
```

IMPLEMENTATION

Chip Name : **Register (Clocked)** Time : **74**

Input pins		Output pins	
Name	Value	Name	Value
in[16]	32767	out[16]	32767
load	1		

HDL

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/03/a/Register.nasm

/**
 * 16-bit register:
 * If load[t] == 1 then out[t+1] = in[t]
 * else out does not change
 */
CHIP Register {
    IN in[16], load;
    OUT out[16];
```

Internal pins

Name	Value
------	-------

```
set load 1,
tick,
output;

tock,
output;

set in %B1011111111111111,
set load 0,
tick,
output;

tock,
output;

set load 1,
tick,
output;

tock,
output;

set in %B0111111111111111,
set load 0,
tick,
output;

tock,
output;

set load 1,
tick,
output;

tock,
output;
```

End of script - Comparison ended successfully

PC(PROGRAM COUNTER)

HDL CODE

```
CHIP PC {
    IN in[16],load,inc,reset;
    OUT out[16];

    PARTS:
        // Put your code here:
        Inc16(in=FBout,out=incout);

        Mux16(a=false,b=incout,sel=inc,out=w0);
        Mux16(a=w0,b=in,sel=load,out=w1);
        Mux16(a=w1,b=false,sel=reset,out=cout);

        Or3input(a=inc,b=load,c=reset,out=regload);

        Register(in=cout,load=regload,out=out,out=FBout);
}
```

IMPLEMENTATION

Chip Name :

Time :

Input pins		Output pins	
Name	Value	Name	Value
in[16]	22222	out[16]	0
load	0		
inc	0		
reset	1		

HDL

```
// This file is part of www.nanc
// and the book "The Elements of
// by Nisan and Schocken, MIT Pr
// File name: projects/03/a/PC.t

/**
 * A 16-bit counter with load ar
 * if (reset[t] == 1) out[t]
 * else if (load[t] == 1) out[t]
 * else if (inc[t] == 1) out[t]
 * else out[t]
 */

CHIP PC {
```

Internal pins

Name	Value
FBout[16]	0
incout[16]	1
w0[16]	0
w1[16]	0
cout[16]	0
regload	1

```
tock,
output;

set reset 1,
tick,
output;

tock,
output;

set in 0,
set reset 0,
set load 1,
tick,
output;

tock,
output;

set load 0,
set inc 1,
tick,
output;

tock,
output;

set in 22222,
set reset 1,
set inc 0,
tick,
output;

tock,
output;
```

End of script - Comparison ended successfully

INBUILT CHIPS FOR SCREEN AND KEY:

CHIP Keyboard {

OUT out[16]; // The ASCII code of the pressed key,

// or 0 if no key is currently pressed,

// or one the special codes listed in Figure 5.5.

BUILTIN Keyboard;

}

CHIP Screen {

IN in[16], // what to write

load, // write-enable bit

address[13]; // where to read/write

OUT out[16]; // Screen value at the given address

BUILTIN Screen;

CLOCKED in, load;

}

MEMORY

HDL CODE

```
CHIP Memory {
  IN in[16], load, address[15];
  OUT out[16];

  PARTS:
    // Put your code here:
    DMux4Way(in=load, sel=address[13..14], a=loadram1, b=loadram2, c=loadscreen, d=loadkbd);
    Or(a=loadram1, b=loadram2, out=loadram);
    RAM16K(in=in, load=loadram, address=address[0..13], out=ramout);
    Screen(in=in, load=loadscreen, address=address[0..12], out=scrout);
    Keyboard(out=kbout);
    Mux4Way16(a=ramout, b=ramout, c=scrout, d=kbout, sel=address[13..14], out=out);
}
```

IMPLEMENTATION

Chip Name : **Memory (Clocked)** Time : **331364**

Input pins		Output pins	
Name	Value	Name	Value
in[16]	-1	out[16]	0
load	0		
address[15]	24576		

HDL

```
* Screen and Keyboard chip spec
*/

CHIP Memory {
  IN in[16], load, address[15];
  OUT out[16];

  PARTS:
    // Put your code here:
    DMux4Way(in=load, sel=address[13..14], a=loadram1, b=loadram2, c=loadscreen, d=loadkbd);
    Or(a=loadram1, b=loadram2, out=loadram);
    RAM16K(in=in, load=loadram, address=address[0..13], out=ramout);
    Screen(in=in, load=loadscreen, address=address[0..12], out=scrout);
    Keyboard(out=kbout);
    Mux4Way16(a=ramout, b=ramout, c=scrout, d=kbout, sel=address[13..14], out=out);
}
```


Internal pins

Name	Value
loadram1	0
loadram2	0
loadscreen	0
loadkbd	0
loadram	0
ramout[16]	2222
scrout[16]	0
kbout[16]	0

RAM 16K:

8189	0
8190	0
8191	0
8192	2222
8193	0
8194	0
8195	0

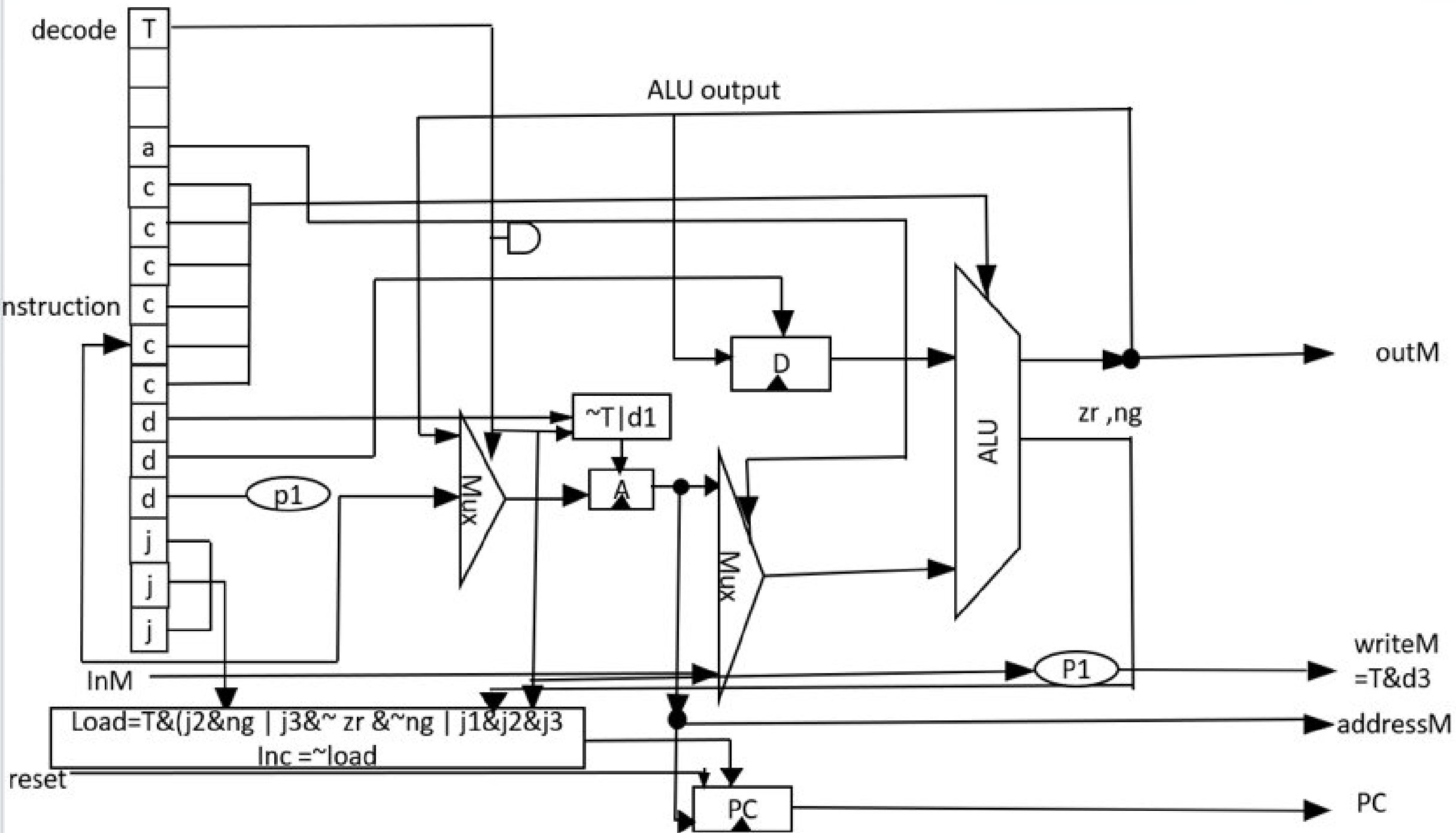End of script - Comparison ended successfully



CPU abstraction


A chip that implements the Hack IS:

A instruction Symbolic: @xxx (xxx is a decimal value ranging from 0 to 32767, or a symbol bound to such a decimal value)
Binary: 0 vvvvvvvvvvvvvvvvv (vv ... v = 15-bit value of xxx)

C instruction Symbolic: dest = comp; jump (comp is mandatory.
If dest is empty, the = is omitted;
If jump is empty, the ; is omitted)
Binary: 111acccccddjjj

comp	c c c c c c	dest	d d d	Effect: store comp in:
0	1 0 1 0 1 0	null	0 0 0	the value is not stored
1	1 1 1 1 1 1	M	0 0 1	RAM[A]
-1	1 1 1 0 1 0	D	0 1 0	D register (reg)
D	0 0 1 1 0 0	DM	0 1 1	RAM[A] and D reg
A	M 1 1 0 0 0 0	A	1 0 0	A reg
!D	0 0 1 1 0 1	AM	1 0 1	A reg and RAM[A]
!A	!M 1 1 0 0 0 1	AD	1 1 0	A reg and D reg
-D	0 0 1 1 1 1	ADM	1 1 1	A reg, D reg, and RAM[A]
-A	-M 1 1 0 0 1 1			
D+1	0 1 1 1 1 1	jump	j j j	Effect:
A+1	M+1 1 1 0 1 1 1	null	0 0 0	no jump
D-1	0 0 1 1 1 0	JGT	0 0 1	if comp > 0 jump
A-1	M-1 1 1 0 0 1 0	JEQ	0 1 0	if comp = 0 jump
D+A	D+M 0 0 0 0 1 0	JGE	0 1 1	if comp ≥ 0 jump
D-A	D-M 0 1 0 0 1 1	JLT	1 0 0	if comp < 0 jump
A-D	M-D 0 0 0 1 1 1	JNE	1 0 1	if comp ≠ 0 jump
D&A	D&M 0 0 0 0 0 0	JLE	1 1 0	if comp ≤ 0 jump
D A	D M 0 1 0 1 0 1	JMP	1 1 1	unconditional jump

a == 0 a == 1

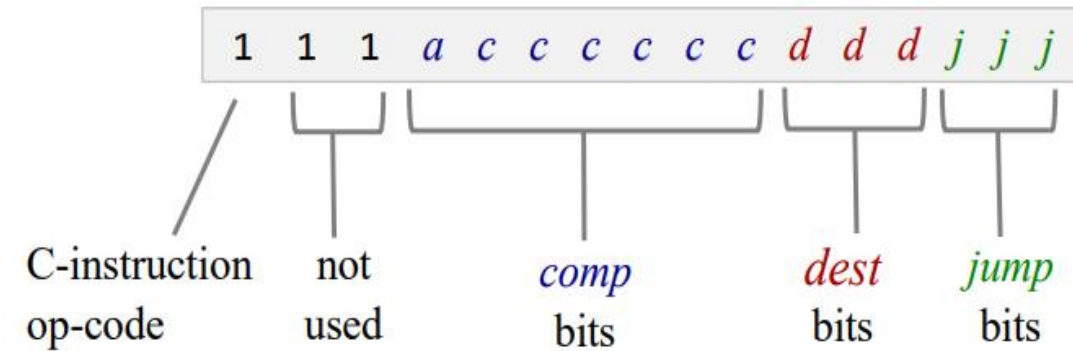

HDL CODE

```
CHIP CPU {  
  
    IN inM[16],          // M value input (M = contents of RAM[A])  
        instruction[16], // Instruction for execution  
        reset;           // Signals whether to re-start the current  
                          // program (reset==1) or continue executing  
                          // the current program (reset==0).  
  
    OUT outM[16],        // M value output  
        writeM,          // Write to M?  
        addressM[15],    // Address in data memory (of M)  
        pc[15];          // address of next instruction  
  
    PARTS:  
        Not(in=instruction[15], out=Ainstruction);  
        Not(in=Ainstruction, out=Cinstruction);  
        And(a=Cinstruction, b=instruction[5], out=ALUtoA);  
        Mux16(a=instruction, b=ALUout, sel=ALUtoA, out=Aregin);  
        Or(a=Ainstruction, b=ALUtoA, out=loadA);  
        ARegister(in=Aregin, load=loadA, out=Aout);  
        Mux16(a=Aout, b=inM, sel=instruction[12], out=AMout);  
        And(a=Cinstruction, b=instruction[4], out=loadD);  
        DRegister(in=ALUout, load=loadD, out=Dout);  
        ALU(x=Dout, y=AMout, zx=instruction[11], nx=instruction[10], zy=instruction[9], ny=instruction[8], f=instruction[7], no=instruction[6], out=ALUout, zr=ZRout, ng=NGout);  
        Or16(a=false, b=Aout, out[0..14]=addressM);  
        Or16(a=false, b=ALUout, out=outM);  
        And(a=Cinstruction, b=instruction[3], out=writeM);  
        And(a=ZRout, b=instruction[1], out=jeq);  
        And(a=NGout, b=instruction[2], out=jlt);  
        Or(a=ZRout, b=NGout, out=zeroOrNeg);  
        Not(in=zeroOrNeg, out=positive);  
        And(a=positive, b=instruction[0], out=jgt);  
        Or(a=jeq, b=jlt, out=jle);  
        Or(a=jle, b=jgt, out=jumpToA);  
        And(a=Cinstruction, b=jumpToA, out=PCload);  
        Not(in=PCload, out=PCinc);  
        PC(in=Aout, inc=PCinc, load=PCload, reset=reset, out[0..14]=pc);  
}
```

CHIP CPU {

IN inM[16], // M value input (M = contents of RAM[A])

instruction[16], // Instruction for execution

reset; // Signals whether to re-start the current
// program (reset==1) or continue executing
// the current program (reset==0).

OUT outM[16], // M value output

writeM, // Write to M?

addressM[15], // Address in data memory (of M)

pc[15]; // address of next instruction

PARTS:

//to check if the instruction is A-instruction

Not(in=instruction[15], out=Ainstruction); //A-instruction

Not(in=Ainstruction, out=Cinstruction); //C-instruction(opposite)

//to check if the instruction is C-instruction

And(a=Cinstruction, b=instruction[5], out=ALUtoA); // C-instruction

Mux16(a=instruction, b=ALUout, sel=ALUtoA, out=Aregin); // stores the value in A register

//if A-instruction or ALU output to the A register,loadA

Or(a=Ainstruction, b=ALUtoA, out=loadA);

ARegister(in=Aregin, load=loadA, out=Aout); //generates value into A register

//selects A or M depending on the 12-bit instruction value

Mux16(a=Aout, b=inM, sel=instruction[12], out=AMout);

And(a=Cinstruction, b=instruction[4], out=loadD);*// if ALU output is loaded to the D-register*

DRegister(in=ALUout, load=loadD, out=Dout); *// loads the value of D-register from ALU*

//calculates the computations

ALU(x=Dout, y=AMout, zx=instruction[11], nx=instruction[10], zy=instruction[9], ny=instruction[8], f=instruction[7], no=instruction[6], out=ALUout, zr=ZRout, ng=NGout);

//decides if cpu can write on data

Or16(a=false, b=Aout, out[0..14]=addressM);*//address to write*

Or16(a=false, b=ALUout, out=outM);*//content in the data memory*

And(a=Cinstruction, b=instruction[3], out=writeM);*//write the data memory*

//determines the jump conditions

And(a=ZRout, b=instruction[1], out=jeq); //zero?jump if zero

And(a=NGout, b=instruction[2], out=jlt); //negative ?jump if negative

Or(a=ZRout, b=NGout, out=zeroOrNeg); //negative or zero?

Not(in=zeroOrNeg, out=positive); // positive(not zero nor negative)

And(a=positive, b=instruction[0], out=jgt);

Or(a=jeq, b=jlt, out=jle);

Or(a=jle, b=jgt, out=jumpToA);

And(a=Cinstruction, b=jumpToA, out=PCload); //load pc if c-instruction and conditions met

Not(in=PCload, out=PCinc); //increment only if the pc is not loaded

PC(in=Aout, inc=PCinc, load=PCload, reset=reset, out[0..14]=pc);

}

IMPLEMENTATION

Chip Name : CPU (Clocked)

Time : 48

Input pins		Output pins	
Name	Value	Name	Value
inM[16]	11111	outM[16]	1
instruction[16]	32767	writeM	0
reset	0	addressM[15]	32767
		pc[15]	1

HDL

```

CHIP CPU {
    IN  inM[16],          // M va
        instruction[16], // Inst
        reset;           // Sigr
                        // proq
                        // the

    OUT outM[16],         // M va
        writeM,           // Writ
        addressM[15],     // Addr
        pc[15];           // addr

    PARTS:

```

Internal pins

Name	Value
Ainstruction	1
Cinstruction	0
ALUtoA	0
ALUout[16]	1
Aregin[16]	32767
loadA	1
Aout[16]	32767
AMout[16]	11111
loadD	0
Dout[16]	1
ZRout	0
NGout	0
jeq	0

```

set instruction %B1110001100000110, // D;JLE
tick, output, tock, output;

set instruction %B1110001100000111, // D;JMP
tick, output, tock, output;

set instruction %B11101111111010000, // D=1
tick, output, tock, output;

set instruction %B11100011000000001, // D;JGT
tick, output, tock, output;

set instruction %B11100011000000010, // D;JEQ
tick, output, tock, output;

set instruction %B11100011000000011, // D;JGE
tick, output, tock, output;

set instruction %B11100011000000100, // D;JLT
tick, output, tock, output;

set instruction %B11100011000000101, // D;JNE
tick, output, tock, output;

set instruction %B11100011000000110, // D;JLE
tick, output, tock, output;

set instruction %B11100011000000111, // D;JMP
tick, output, tock, output;


set reset 1;
tick, output, tock, output;

set instruction %B01111111111111111, // @32767
set reset 0;
tick, output, tock, output;

```

End of script - Comparison ended successfully

HACK COMPUTER

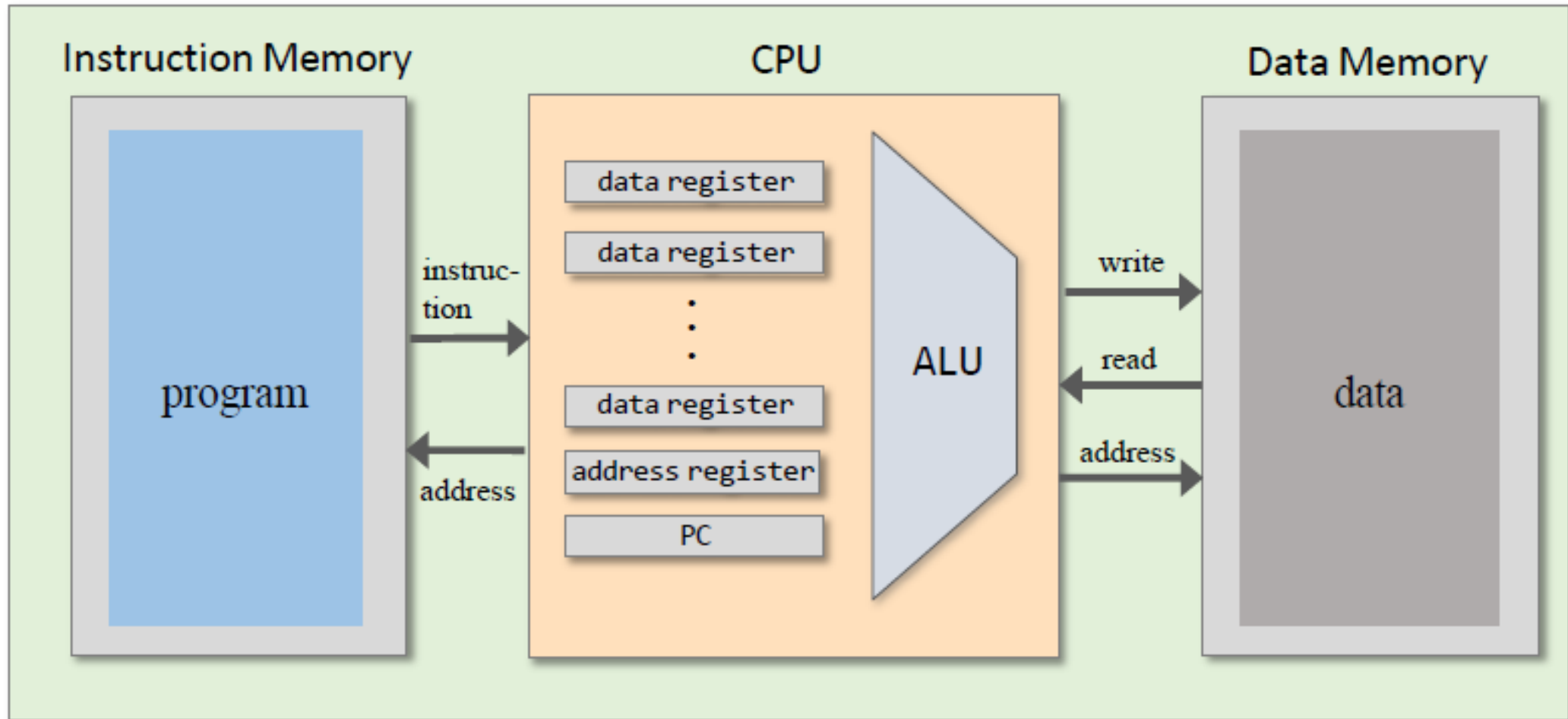

NAND2TETRIS

HDL CODE

```
CHIP Computer {  
  
    IN reset;  
  
    PARTS:  
    // Put your code here:  
    ROM32K(address=pc, out=instruction);  
    CPU(inM=memOut, instruction=instruction, reset=reset, outM=outM,  
        writeM=writeM, addressM=addressM, pc=pc);  
    Memory(in=outM, load=writeM, address=addressM, out=memOut);  
}
```

IMPLEMENTATION

The screenshot displays the NAND2TETRIS implementation interface. The top toolbar includes icons for simulation control (play, step, stop, reset, etc.) and a speed slider. The main interface is divided into several sections:

- Chip Name:** Computer (Clocked) | **Time:** 63
- Input pins:** A table with columns Name and Value. The 'reset' pin has a value of 0.
- Output pins:** A table with columns Name and Value. It is currently empty.
- HDL:** A text area containing the HDL code for the Computer chip. The code is identical to the one shown in the HDL CODE section.
- Internal pins:** A table with columns Name and Value. The values are: pc[15] (24), instruction[16] (-5497), memOut[16] (0), outM[16] (0), writeM (0), and addressM[15] (23).
- RAM 16K:** A table with columns Address and Value. The values are: 20 (0), 21 (0), 22 (0), 23 (0), 24 (0), 25 (0), 26 (0).
- ROM:** A table with columns Address and Value. The values are: 18 (1110001100001000), 19 (0000000000010000), 20 (1111110010011000), 21 (0000000000001010), 22 (1110001100000001), 23 (0000000000010111), 24 (1110101010000111).
- ALU:** A section showing the ALU output. The D Input is 0, the M/A Input is 23, and the ALU output is 0.

End of script - Comparison ended successfully


PART B:

Synchronous down counter from 9 onwards to 0

INTRODUCTION

- A synchronous counter is a type of digital counter circuit in which all flip-flops or stages change state simultaneously in response to a clock signal.
- The most common types of synchronous counters are binary counters, where each flip-flop represents a binary digit in the counting sequence.
- A down counter is a type of digital counter circuit that counts down from a predetermined value to zero
- Down counters are commonly implemented using flip-flops and combinational logic circuits.

State diagram

 

TRUTH TABLE

Q4	Q3	Q2	Q1	Q4*	Q3*	Q2*	Q1*	T4	T3	T2	T1
0	0	0	0	1	0	0	1	1	0	0	1
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	1	0	0	1	1
0	0	1	1	0	0	1	0	0	0	0	1
0	1	0	0	0	1	1	1	0	1	1	1
0	1	0	1	0	1	0	0	0	0	0	1
0	1	1	0	0	1	0	1	0	0	1	1
0	1	1	1	0	1	1	0	0	0	0	1
1	0	0	0	1	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	0	0	1

K-MAP

For T4:

$Q^3Q^4 \backslash Q^1Q^2$	00	01	11	10
00	1			
01				
11	x	x	x	x
10	1		x	x

$$= Q1'Q2'Q3'$$

For T3:

$Q^3Q^4 \backslash Q^1Q^2$	00	01	11	10
00				
01	1			
11	x	x	x	x
10	1		x	x

$$= Q3Q2'Q1' + Q4Q2'Q1'$$

For T2:

$Q^3Q^4 \backslash Q^1Q^2$	00	01	11	10
00				1
01	1			1
11	x	x	x	x
10	1		x	x


$$= Q2Q1' + Q3Q2'Q1' + Q4Q2'Q1'$$

For T1:

$Q^3Q^4 \backslash Q^1Q^2$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	X	X	X	X
10	1	X	X	X

$$= 1$$

BLOCK DIAGRAM

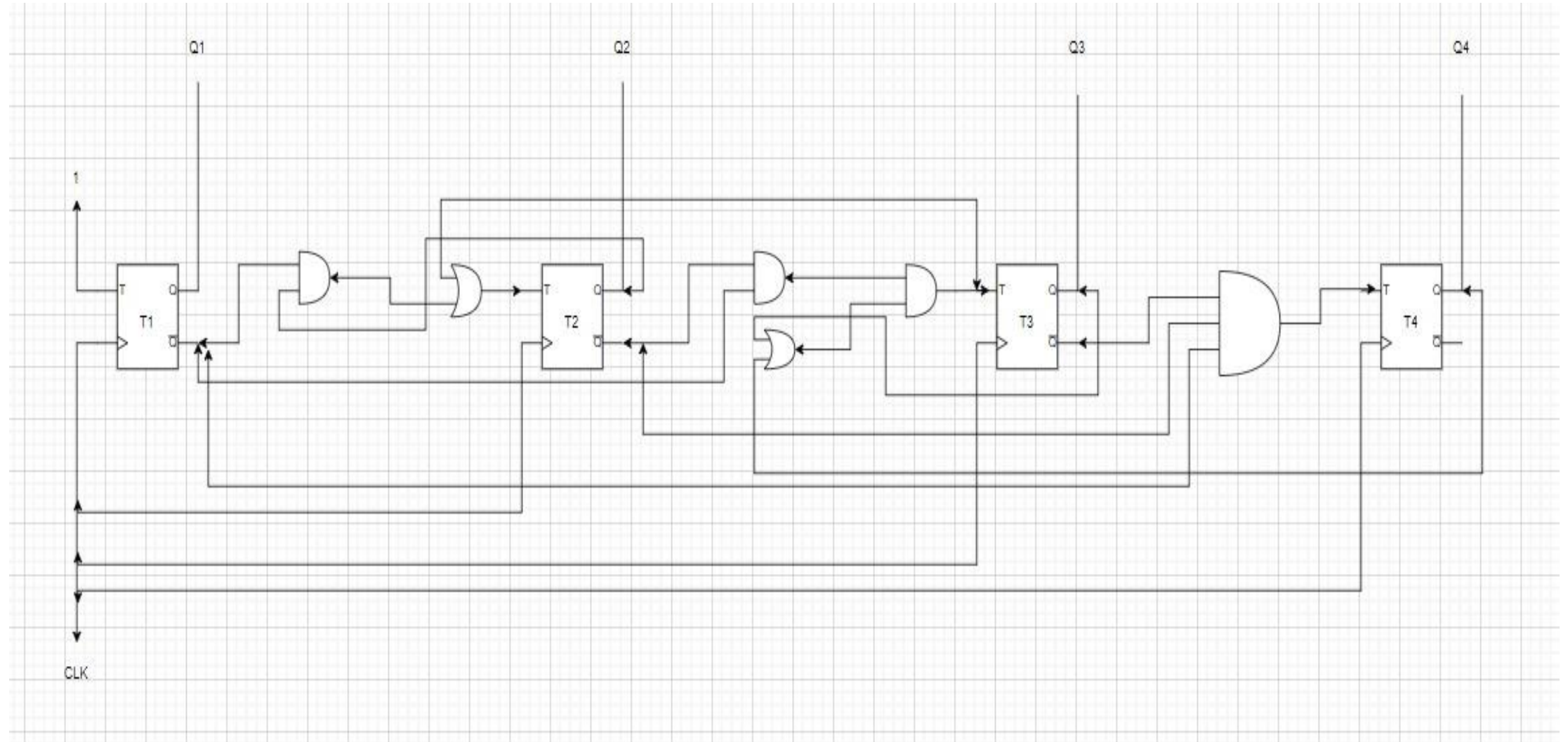

IMPLEMENTATION

And 3 input

```
CHIP And3in{
  IN a,b,c;
  OUT out;
  PARTS:
    And(a=a,b=b,out=o1);
    And(a=o1,b=c,out=out);
}
```

T Flip Flop

```
CHIP TFF {
  IN T;
  OUT out;
  PARTS:
    Xor(a = T, b = dffout, out = xout);
    DFF(in = xout, out = dffout, out=out);
}
```

Or 3 input

```
CHIP Or3in{
  IN a,b,c;
  OUT out;
  PARTS:
    //Put your code here:
    Or(a=a,b=b,out=o1);
    Or(a=o1,b=c,out=out);
}
```

HDL CODE

```
CHIP Mod10counter1
{
    OUT q[4];

    PARTS:

        TFF(T = TA, out = q[3], out = qa);
        And3in(a = nqd, b = nqc, c = nqb, out = TA);

        TFF(T = TB, out = q[2], out = qb);
        And3in(a=qb,b=nqc,c=nqd,out=a1);
        And3in(a=qa,b=nqc,c=nqd,out=a2);
        Or(a=a1,b=a2,out=TB);

        TFF(T = TC, out = q[1], out = qc);
        And(a=qc,b=nqd,out=a3);
        Or(a=TB,b=a3,out=TC);

        TFF(T = true, out = q[0], out = qd);

        Not(in = qa, out = nqa);
        Not(in = qb, out = nqb);
        Not(in = qc, out = nqc);
        Not(in = qd, out = nqd);
}
```

IMPLEMENTATION

Chip Name : Mod10counter1 (Clocked)		Time : 81	
Input pins		Output pins	
Name	Value	Name	Value
		q[4]	9
HDL		Internal pins	
And3in(a=qa,b=nqc,c=nqd,out=a2); Or(a=a1,b=a2,out=TB); TFF(T = TC, out = q[1], out = qc); And(a=qc,b=nqd,out=a3); Or(a=TB,b=a3,out=TC); TFF(T = true, out = q[0], out = qd); Not(in = qa, out = nqa); Not(in = qb, out = nqb); Not(in = qc, out = nqc); Not(in = qd, out = nqd); }			
		Name	Value
		TA	0
		qa	1
		nqd	0
		nqc	1
		nqb	1
		TB	0
		qb	0
		a1	0
		a2	0
		TC	0
		qc	0
		a3	0
		qd	1

CONCLUSION

- In summary, our investigation has led to the development and examination of a 4-bit synchronous down counter engineered to count in a decrementing sequence from 9 to 0. Employing four flip-flops to represent individual digits, the synchronous design guarantees simultaneous state changes across all flipflops with each clock pulse. The counter initiates at 1001(9) and successively transitions through binary states, concluding at 0000(0)